

Solutions to *The Art of Electronics 3rd Edition*

February 13, 2024


Contents

1	Solutions for Chapter 3	5		
1.1	Exercise 3.1	5	1.10	Exercise 3.10 10
1.2	Exercise 3.2	5	1.11	Exercise 3.11 TODO: write solution 10
1.3	Exercise 3.3	6	1.12	Exercise 3.12 TODO: write solution 10
1.4	Exercise 3.4	6	1.13	Exercise 3.13 TODO: write solution 10
1.5	Exercise 3.5	6	1.14	Exercise 3.14 TODO: write solution 10
1.6	Exercise 3.6	6	1.15	Exercise 3.15 TODO: write solution 10
1.7	Exercise 3.7	7	1.16	Exercise 3.16 TODO: write solution 10
1.8	Exercise 3.8	8	1.17	Exercise 3.17 TODO: write solution 10
1.9	Exercise 3.9	10	1.18	Exercise 3.18 TODO: write solution 10

Solutions for Chapter 3

Exercise 3.1

Figure 1.1: JFET current source

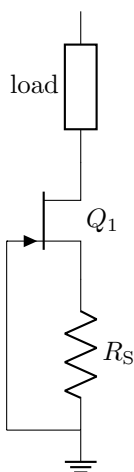

From Figure 3.21 of the book, one can see that a drain current equal to 1 mA corresponds to a gate-source voltage of -0.6 V . Therefore:

$$R_S = \frac{0.6\text{ V}}{1\text{ mA}} = 600\ \Omega$$

Exercise 3.2

At $V_{GS} = V_{G0}$:

$$r_{GS} = r_{G0} = \frac{1}{2k(V_{G0} - V_{th})}$$

The ratio between r_{DS} and R_{G0} returns:

$$\frac{r_{DS}}{r_{G0}} = \frac{2k(V_{G0} - V_{th})}{2k(V_{GS} - V_{th})}$$

Exercise 3.3

Being g_m the differential conductance of the FET operated in aturation region, it can be expressed as:

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{\partial}{\partial V_{GS}} k (V_{GS} - V_{th})^2 = 2k (V_{GS} - V_{th})$$

Therefore:

$$g_m = \frac{1}{r_{DS}}$$

Exercise 3.4

- (a) The voltage across the drain-gate capacitance when the JFET is switched on ($V_{DS} = 0$ V) is equal to 50 V-10 V=40 V. Considering a maximum current across this capacitance equal to 1 mA:

$$t_{ON} = \frac{40 \text{ V } 200 \text{ pF}}{1 \text{ mA}} = 8 \text{ } \mu\text{s}$$

- (b) Since the current is equal to the charge over time, we have:

$$t_{ON} = \frac{40 \text{ nC}}{1 \text{ mA}} = 40 \text{ } \mu\text{s}$$

Exercise 3.5

The 1 pF drain-source capacitance happens to be in series with the 10 k Ω load resistance. The capacitive reactance is:

$$X_{DS} = \frac{1}{2\pi 1 \text{ MHz } 1 \text{ pF}} = 160 \text{ k}\Omega$$



Therefore, the feedthrough is given by:

$$20 \log_{10} \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 160 \text{ k}\Omega} = -25 \text{ dB}$$

Exercise 3.6

In this case, the output 10 k Ω resistance is in parallel with the 50 Ω R_{ON} resistance. Their equivalent resistance is about 50 Ω . Similarly to the previous exercise, the feedthrough is given by:

$$20 \log_{10} \frac{50 \text{ } \Omega}{50 \text{ } \Omega + 160 \text{ k}\Omega} = -70 \text{ dB}$$

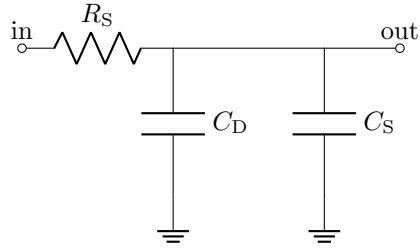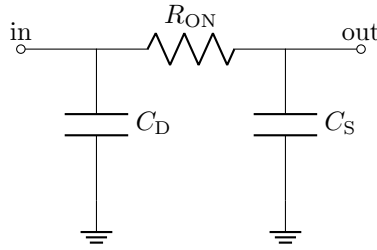Exercise 3.7Figure 1.2: Zero ohm R_{ON} Figure 1.3: $75\ \Omega$ R_{ON} 

For this exercise we assume that the load resistance of $100\ \text{k}\Omega$ does not load the circuit.

- (a) The circuit is that of Figure 1.2. Since $C_D = C_S = C_T = 8\ \text{pF}$, there is a single pole at the frequency f_p :

$$f_p = \frac{1}{4\pi R_S C_T} \approx 1\ \text{MHz}$$

- (b) In this case the circuit is depicted in Figure 1.3. The circuit has one pole at DC and another pole at f_p :

$$f_p = \frac{1}{2\pi R_{ON} C_T} \approx 265\ \text{MHz}$$

Exercise 3.8

Figure 1.4: OFF-OFF

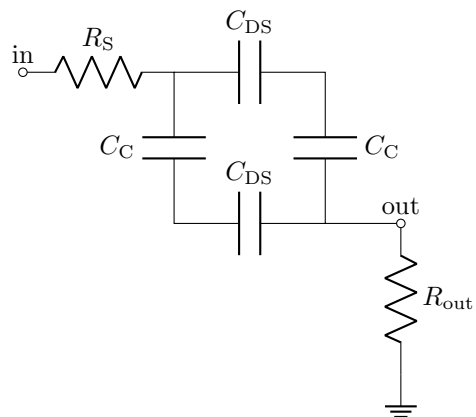


Figure 1.5: OFF-ON

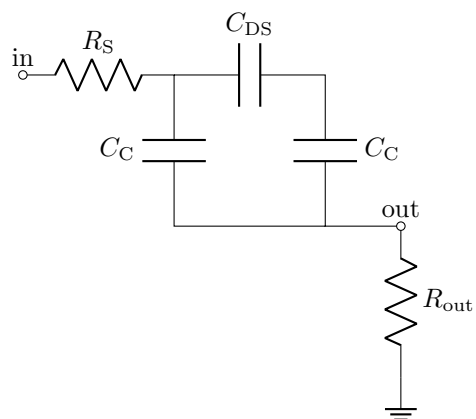


Figure 1.6: ON-OFF


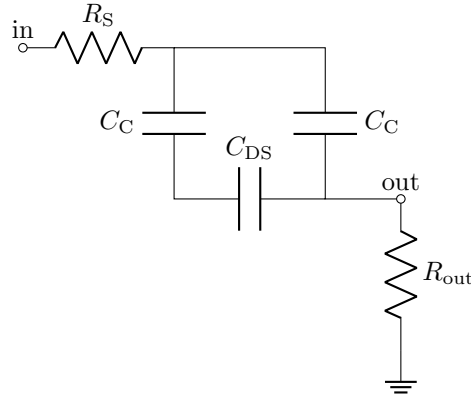


Figure 1.7: ON-ON

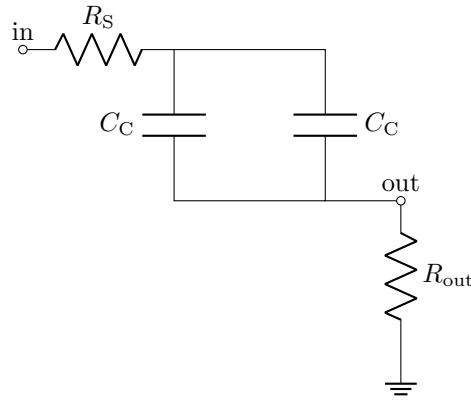

- (a) In this case the reference circuit is depicted in Figure 1.4. The cross-coupling is given by:

$$20 \log_{10} \frac{R_{\text{out}}}{R_{\text{out}} + R_S + 0.5(X_C + X_{\text{DS}})} = -10.75 \text{ dB}$$

being $X_C = \frac{1}{2\pi f C_C} = 320 \text{ k}\Omega$ and $X_{\text{DS}} = \frac{1}{2\pi f C_{\text{DS}}} = 160 \text{ k}\Omega$

- (b) In this case the reference circuit is depicted in Figure 1.5. The cross-coupling is given by:

$$20 \log_{10} \frac{R_{\text{out}}}{R_{\text{out}} + R_S + \frac{X_C(X_C + X_{\text{DS}})}{2X_C + X_{\text{DS}}}} = -9.6 \text{ dB}$$

- (c) In this case the reference circuit is depicted in Figure 1.6. The cross-coupling is the same as before

- (d) In this case the reference circuit is depicted in Figure 1.7. The cross-coupling is given by:

$$20 \log_{10} \frac{R_{\text{out}}}{R_{\text{out}} + R_S + 0.5X_C} = -8.6 \text{ dB}$$

Exercise 3.9

(a) Considering the different combinations of resistors, the -3 dB frequencies can be computed as:

$$f_{3\text{dB},n} = \frac{n G_{10k}}{2\pi C} \quad n = 1 \dots 15$$

where $C = 0.01 \mu\text{F}$ and $G_{10k} = 0.1 \text{ mS}$

(b) The glitch amplitude voltage can be computed as:

$$\Delta V = \frac{20 \text{ pC}}{C} = 2 \text{ mV}$$

Exercise 3.10

The peak output current that the buffer has to provide can be given as the peak time derivative of the output voltage across the 10 nF capacitor multiplied by its value:

$$I_p = 10 \text{ nF} \left. \frac{dV}{dt} \right|_p = 10 \text{ nF} \cdot 2\pi \cdot 10 \text{ kHz} \cdot 1 \text{ V} = 0.6 \text{ mA}$$

Exercise 3.11 **TODO: write solution**

Exercise 3.12 **TODO: write solution**

Exercise 3.13 **TODO: write solution**

Exercise 3.14 **TODO: write solution**

Exercise 3.15 **TODO: write solution**

Exercise 3.16 **TODO: write solution**

Exercise 3.17 **TODO: write solution**

Exercise 3.18 **TODO: write solution**