

Solutions to *The Art of Electronics 3rd Edition*

December 26, 2023


Contents

1	Solutions for Chapter 3	5	1.9	Exercise 3.10	TODO: write solution	6
1.1	Exercise 3.1	5	1.10	Exercise 3.11	TODO: write solution	6
1.2	Exercise 3.3	6	1.11	Exercise 3.12	TODO: write solution	6
1.3	Exercise 3.4	6	1.12	Exercise 3.13	TODO: write solution	6
1.4	Exercise 3.5	6	1.13	Exercise 3.14	TODO: write solution	6
1.5	Exercise 3.6	6	1.14	Exercise 3.15	TODO: write solution	6
1.6	Exercise 3.7	6	1.15	Exercise 3.16	TODO: write solution	6
1.7	Exercise 3.8	6	1.16	Exercise 3.17	TODO: write solution	6
1.8	Exercise 3.9	6	1.17	Exercise 3.18	TODO: write solution	6

Solutions for Chapter 3

Exercise 3.1

Figure 1.1: JFET current source

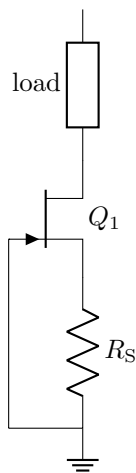

From Figure 3.21 of the book, one can see that a drain current equal to 1 mA corresponds to a gate-source voltage of -0.6 V . Therefore:

$$R_S = \frac{0.6\text{ V}}{1\text{ mA}} = 600\ \Omega$$

Exercise 3.3 **TODO: write solution**

Exercise 3.4 **TODO: write solution**

Exercise 3.5 **TODO: write solution**

Exercise 3.6 **TODO: write solution**

Exercise 3.7 **TODO: write solution**

Exercise 3.8 **TODO: write solution**

Exercise 3.9 **TODO: write solution**

Exercise 3.10 **TODO: write solution**

Exercise 3.11 **TODO: write solution**

Exercise 3.12 **TODO: write solution**

Exercise 3.13 **TODO: write solution**

Exercise 3.14 **TODO: write solution**

Exercise 3.15 **TODO: write solution**

Exercise 3.16 **TODO: write solution**

Exercise 3.17 **TODO: write solution**

Exercise 3.18 **TODO: write solution**